



Mohammadreza
Arani 810196405

Machine project phase 1

Designing a transformer in Simulink,matlab

Due TA:Mr.Dadashi

Teacher:Dr. Abedini



Electrical engineering
University of Tehran



09011690305



babaarani@gamil.com


Due date:15/2/1398

First of all we start by a explanation of the project then we go to Simulink design and at the end answering the questions.


We use 2 sensors at each side of the circuit to discover current and voltage given and driven by the procedure explained in the pdf file given.

4 scopes are used to show the needed information .

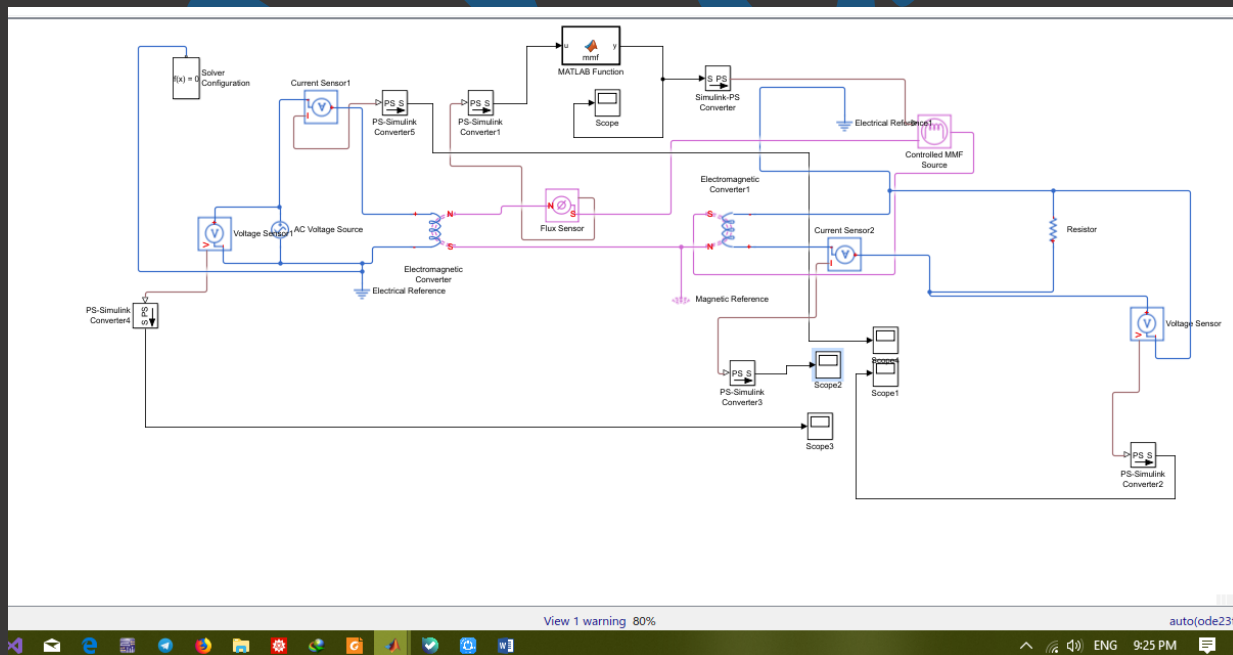Using 180UI core and finding the length and using that in formula $H.L=N.I$ to find $N.I$ and drive it to the circuit.



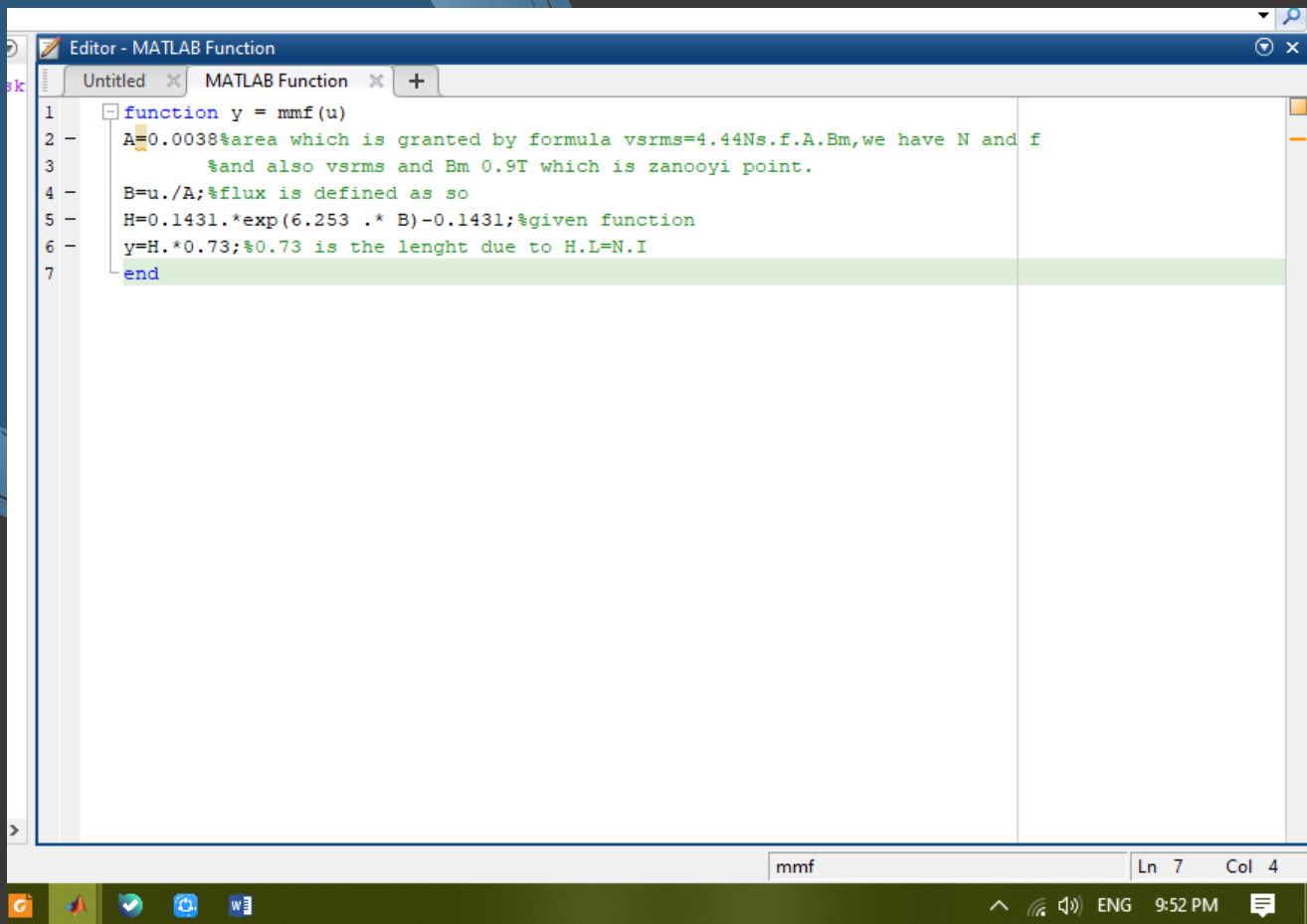The circuit is shown at the top. Flux and voltage and current sensors are used there. flux sensor output is given to matlab function to obtain H which is needed for getting $N.I$.



```
1 function y = mmf(u)
2 A=0.0038;%area which is granted by formula vsrms=4.44Ns.f.A.Bm,we have N and f
3 %and also vsrms and Bm 0.9T which is zanocyi point.
4 B=u./A;%flux is defined as so
5 H=0.1431.*exp(6.253 .* B)-0.1431;%given function
6 y=H.*0.73;%0.73 is the lenght due to H.L=N.I
7 end
```

mmf Ln 7 Col 4


The code in the following page is written to get flux and then calculate the B and then by the formula obtaining the H.

At last $N.I = H.L$ and $L = 0.73$ which I calculated.


$N = 300$ so by the formula we get $A = 0.0038$.

Questions:

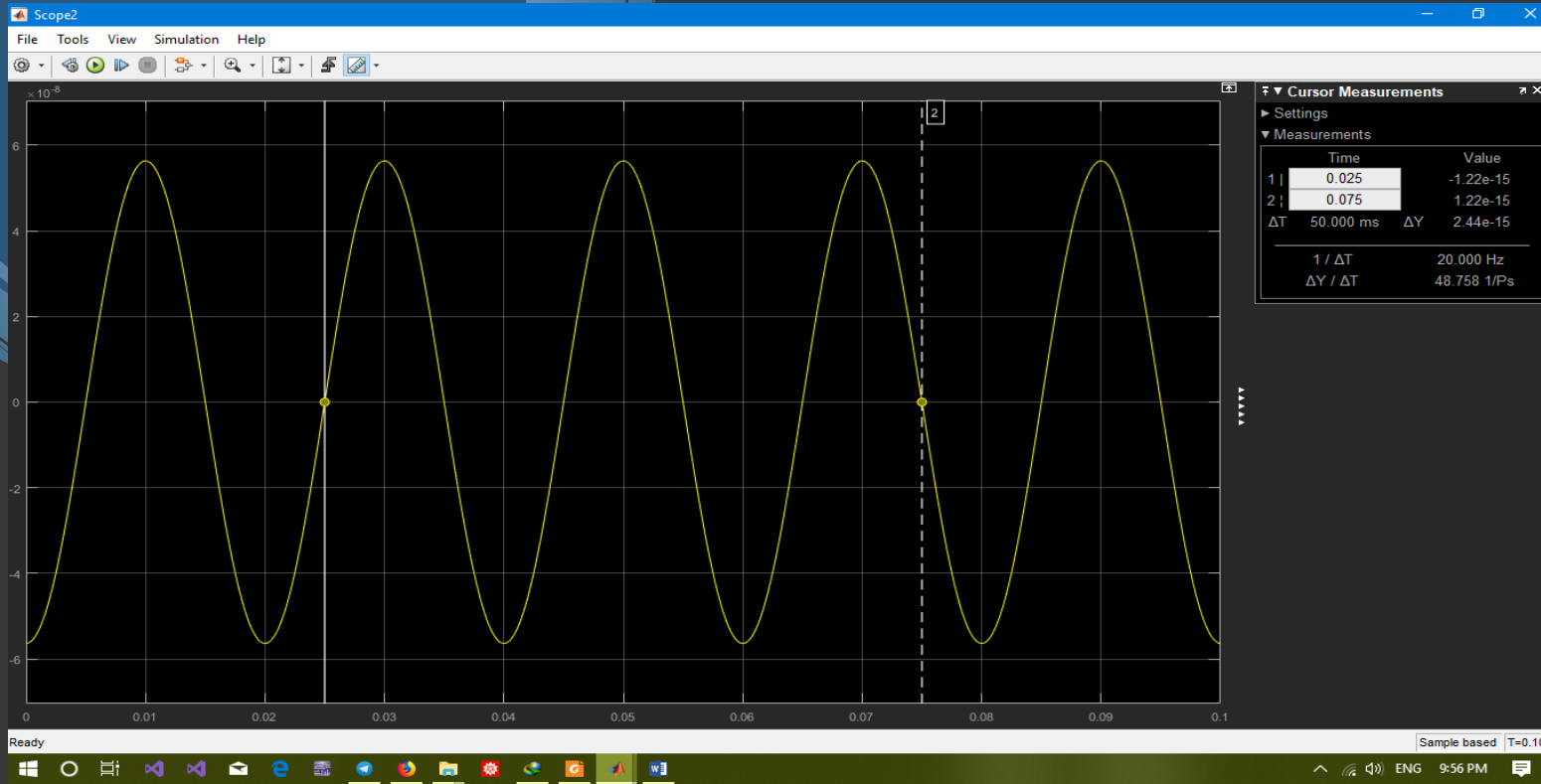1. $R_L = 1 \text{ Gohm} \Rightarrow$ the current:




The flux:

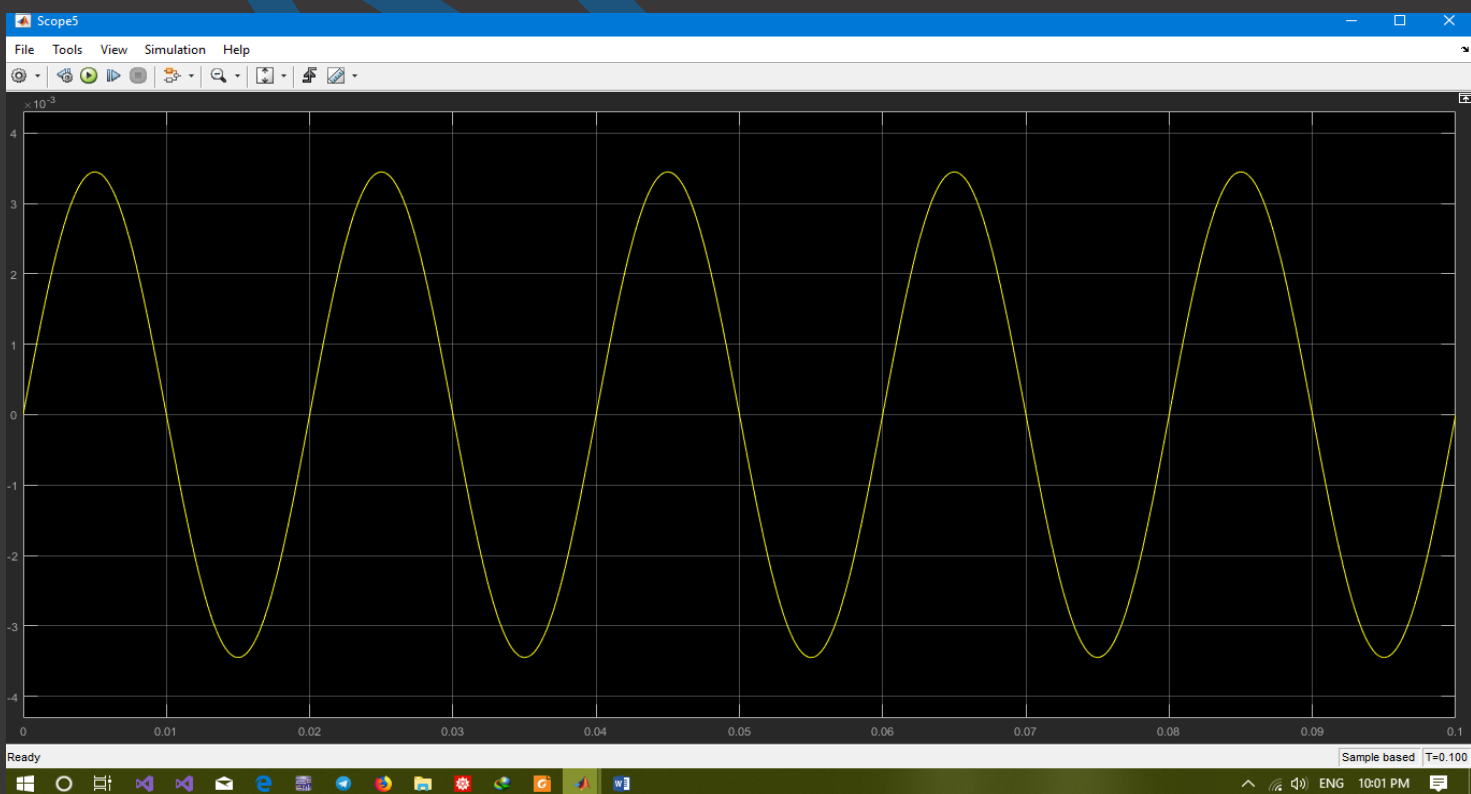


They both seem to be sinoside by the way.

3. Voltage pik is 56.3 in the output and input voltage pik is 325volt and $a=325/56.3=5.77$ which is not our desired a. $230/4=5.75$
We have a bit of diffenence.

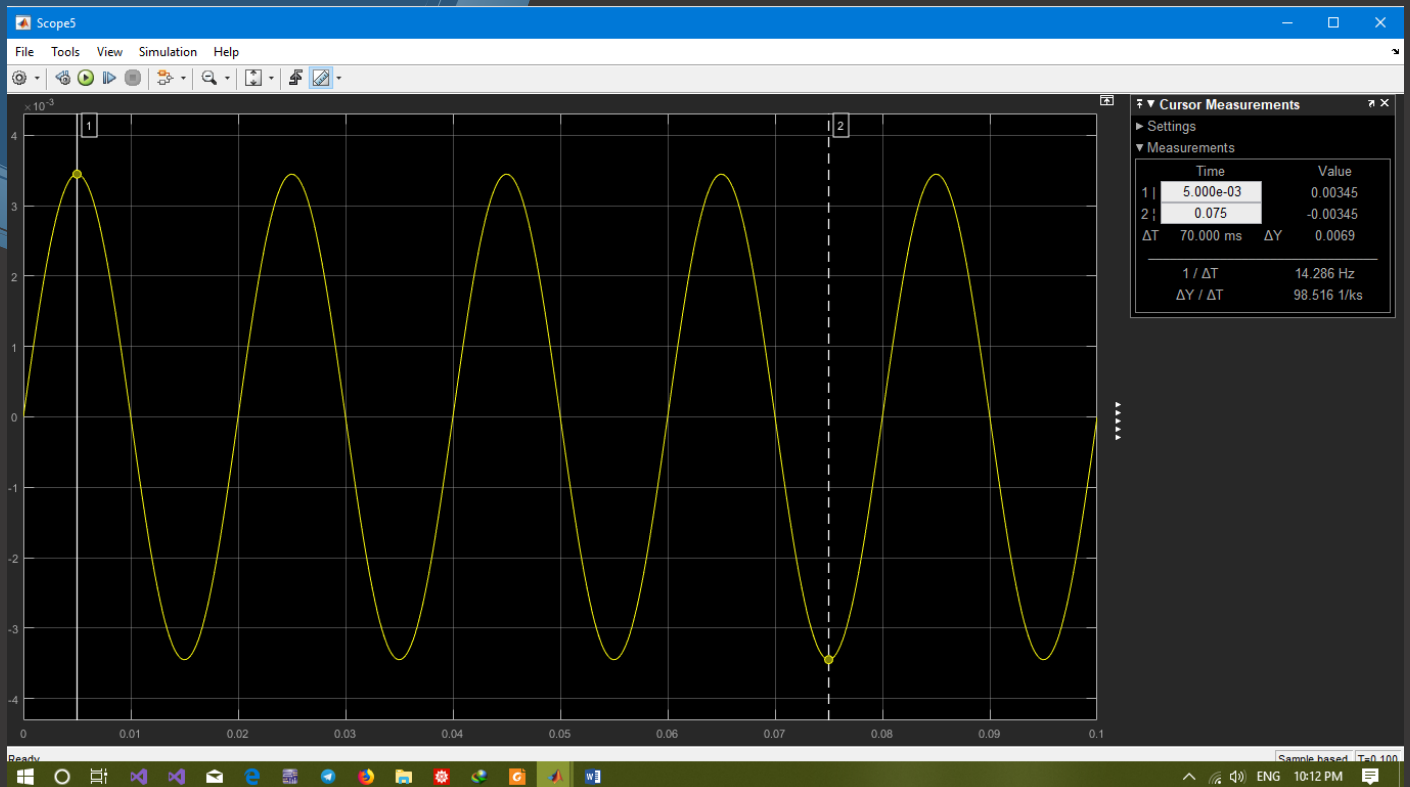
4. Pik of flux is 3.45×10^{-3} so $B_m=0.907$ which is almost equal to $B_m=0.9$ as we desired



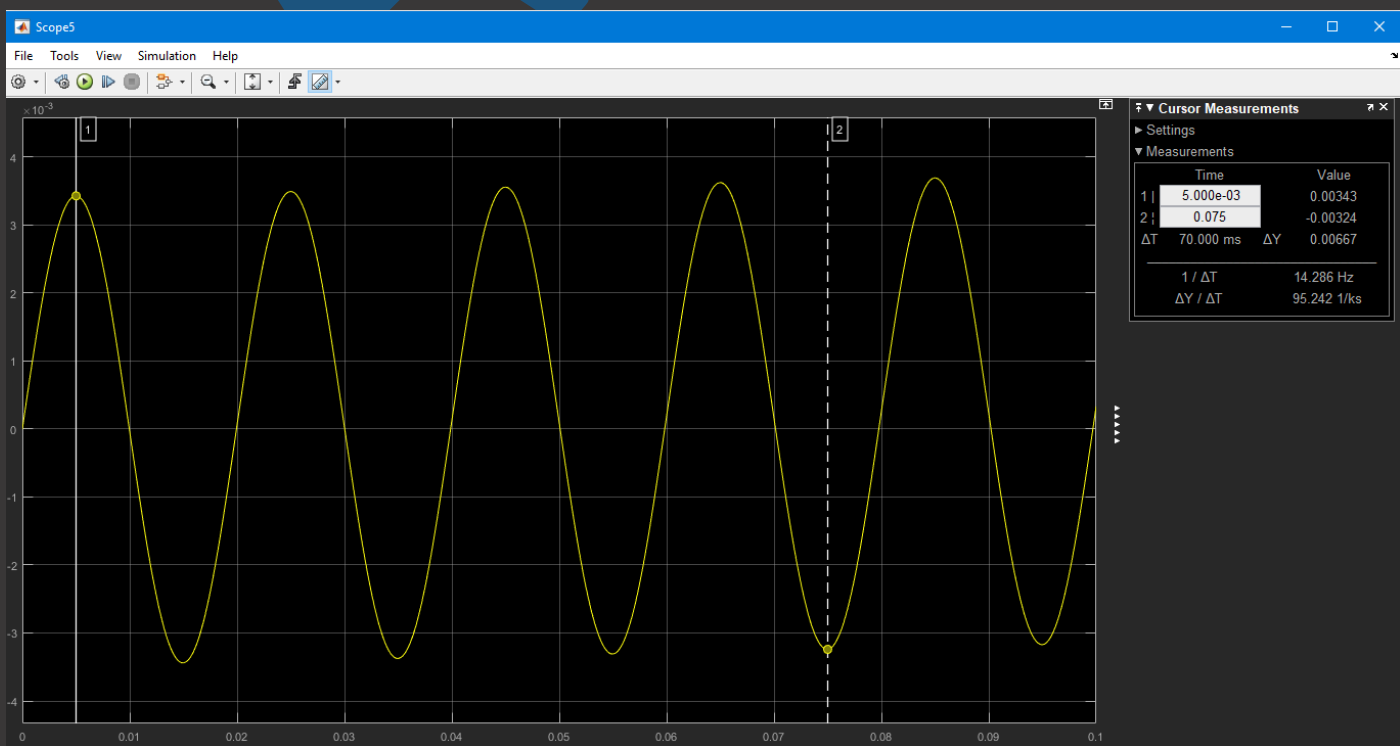5. By applying those resistors we get :
Flux:




Current:

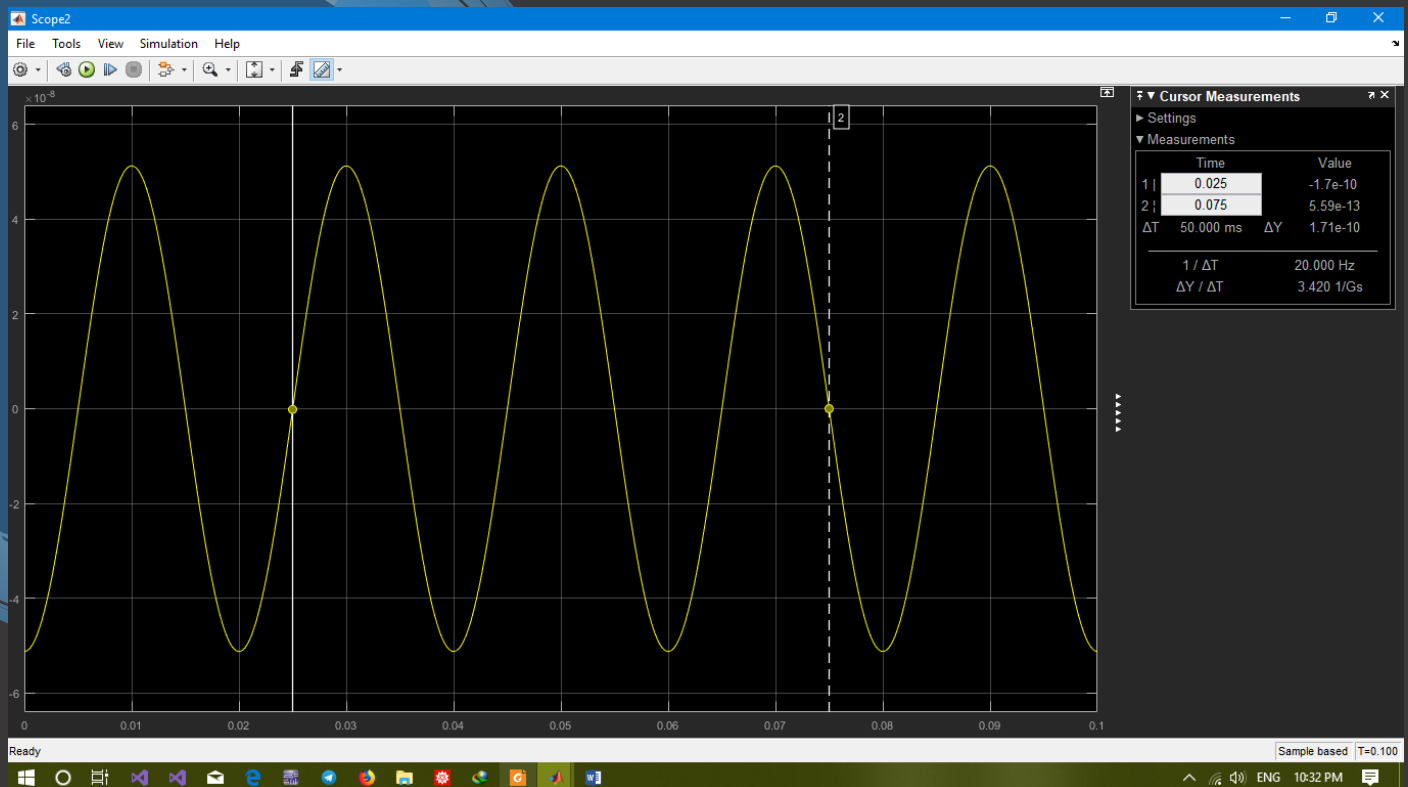


They are still like a sioside

$\Phi = 1/N * (\text{integral of } v \, dt)$ and as v is AC ans sinoside then Φ will look like a sinoside.


6. The current would look like:OUTPUT

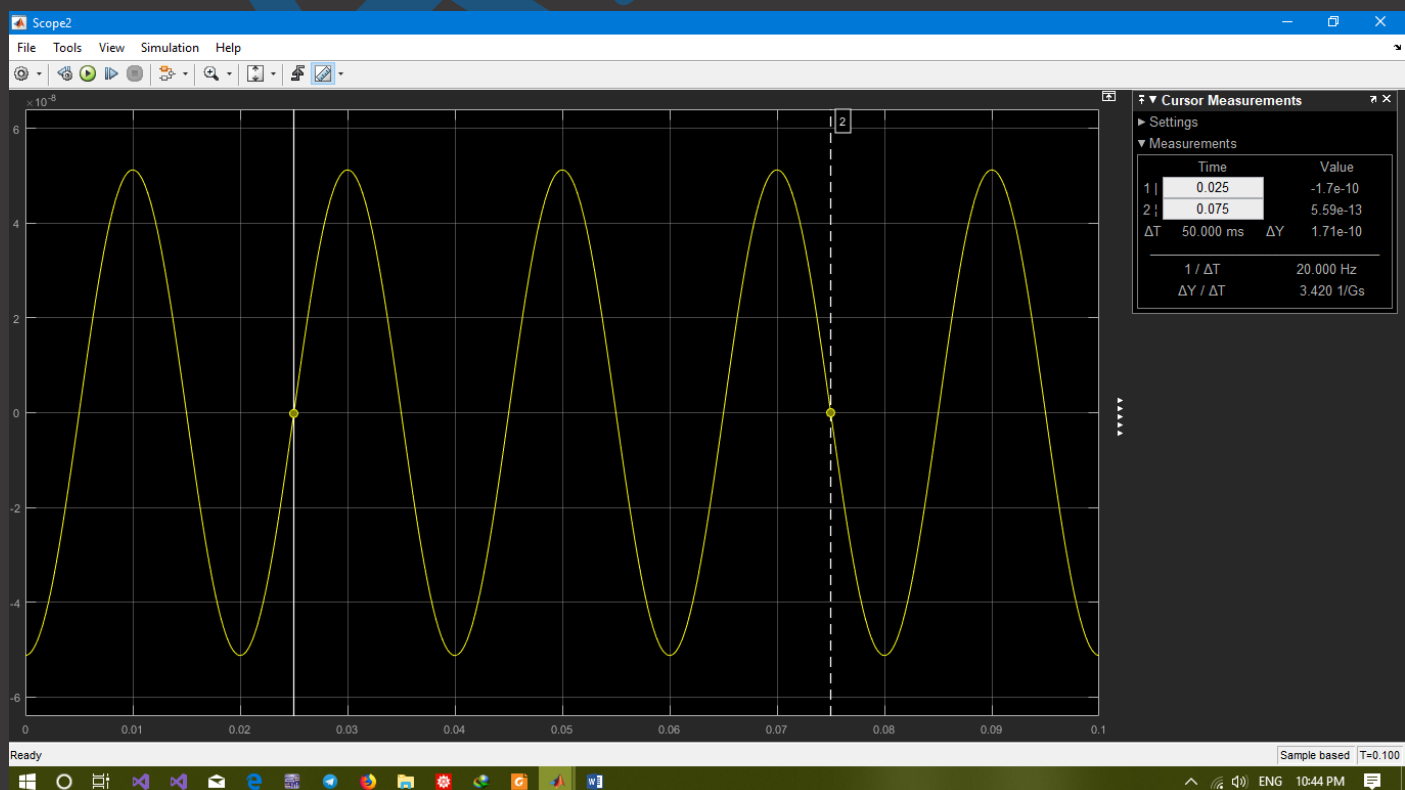


INPUT:

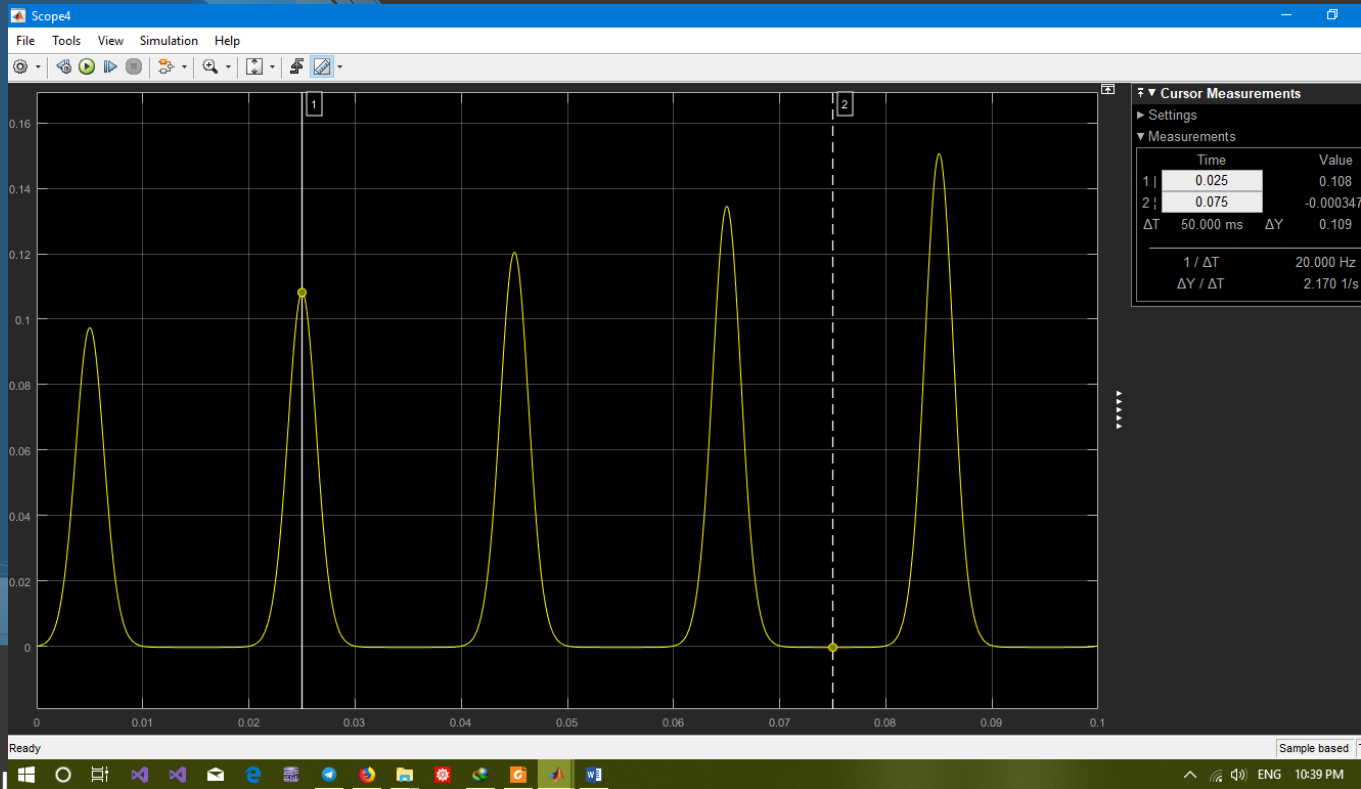

The voltage.
Output:

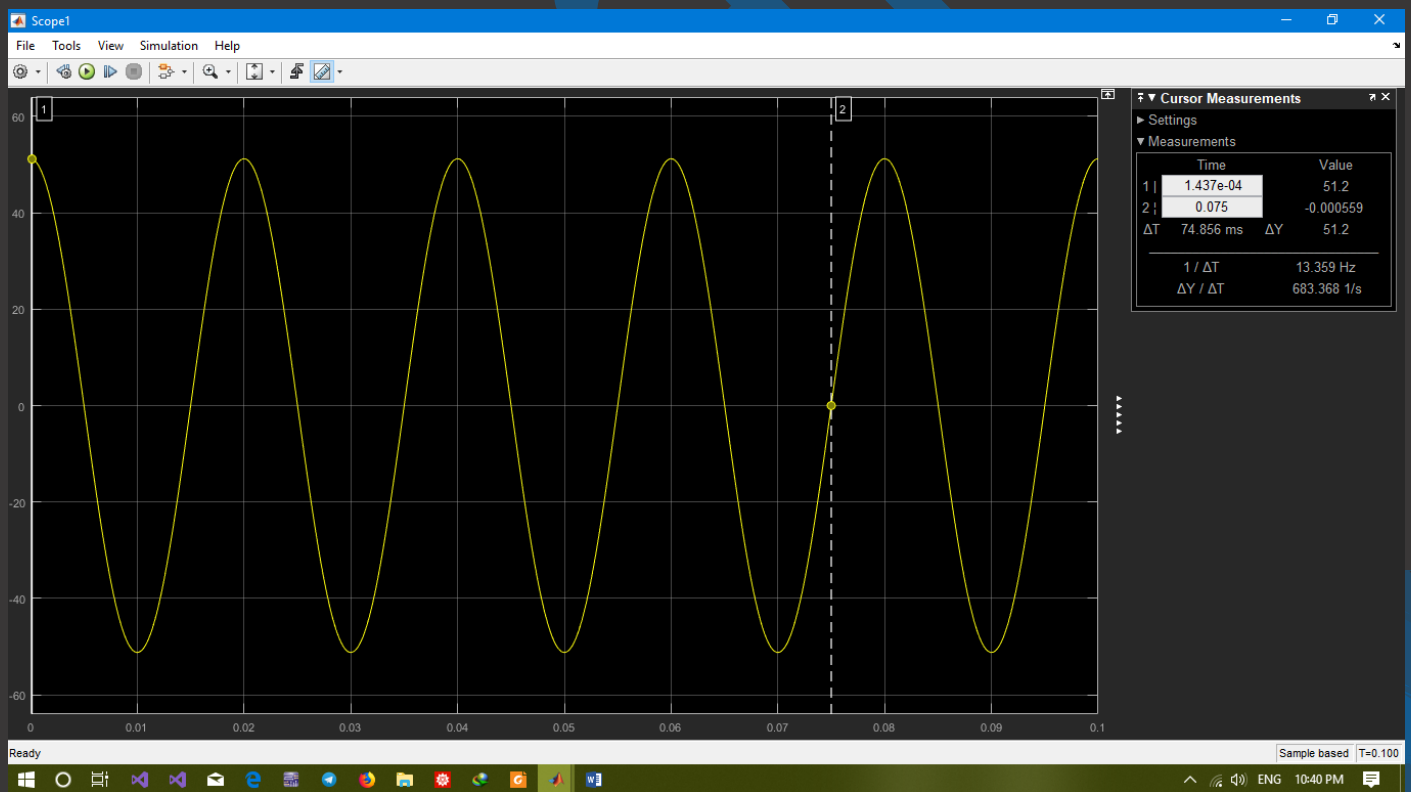

Input:

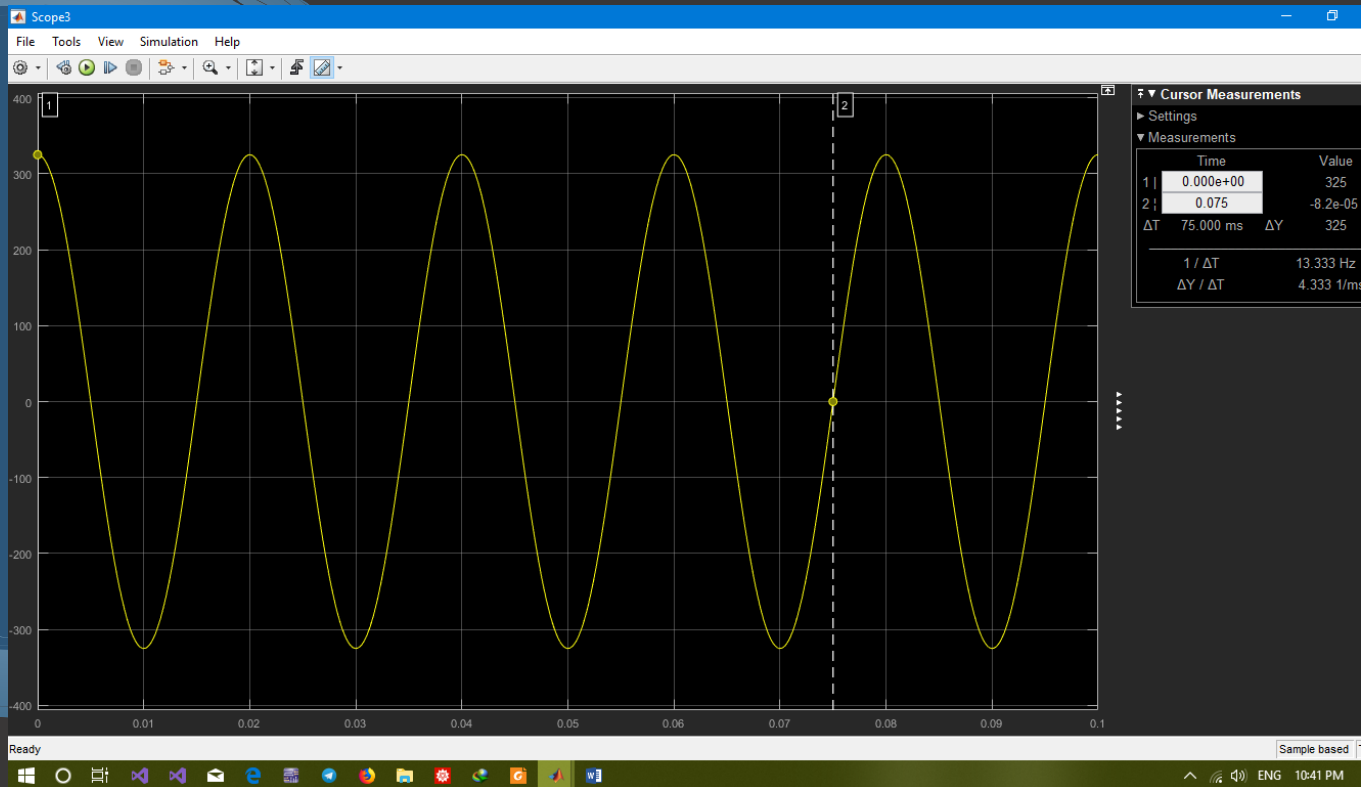

The current is not sinusoidal in the input by changing R_L to 10 ohm. But the voltage remained sinusoidal~!!!

$A = 325 / 51.2 = 6.34$ and it's not equal to what we considered.

7. Lack of time